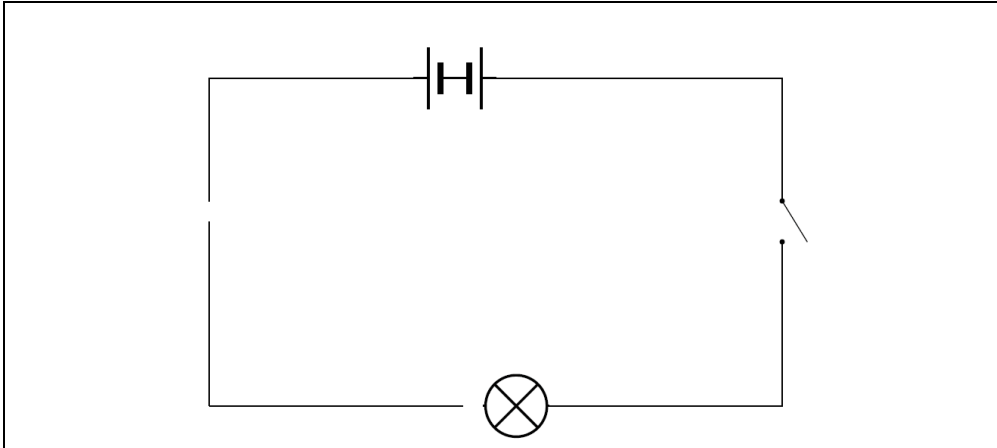


# QUIZ 3

## REVISION ACTIVITY

1. The bulb in the circuit diagram below, does not light up.  
Circle the four parts of the circuit that prevents the bulb from lighting up

[4]



2. Complete the table:

[4]

PARTS	REASONS WHY THE BULB DID NOT LIGHT UP

3. Draw the circuit diagram properly to ensure that the bulb will light up.

[2]

**[TOTAL: 10 Marks]**